



University of Windsor

2nd M.A.Sc. Seminar :

Low Power CMOS Rectifier
and Chien Search Design
for RFID Tags

Presented by: Shu-Yi (Jack) Wong

Introduction

- In noisy automotive environment, Radio Frequency IDentification tags may implement intelligent sensor, which also require extended operating range
- We need robust error correction on the tag and a highly efficient rectifier for power
- BCH code is proven robust and Chien Search is a key part of BCH decoder
- How about differential bridge rectifier?



Overview of The Seminar

- System overview
- 5 slides for Chien search, which is a key part of my initial research effort
- Introducing differential bridge rectifier
- How to get the highest power efficiency?
- Matching for maximum power transfer?
- Parasitic effects and conclusion


System Overview

RFID Reader

RFID Tag




Channel

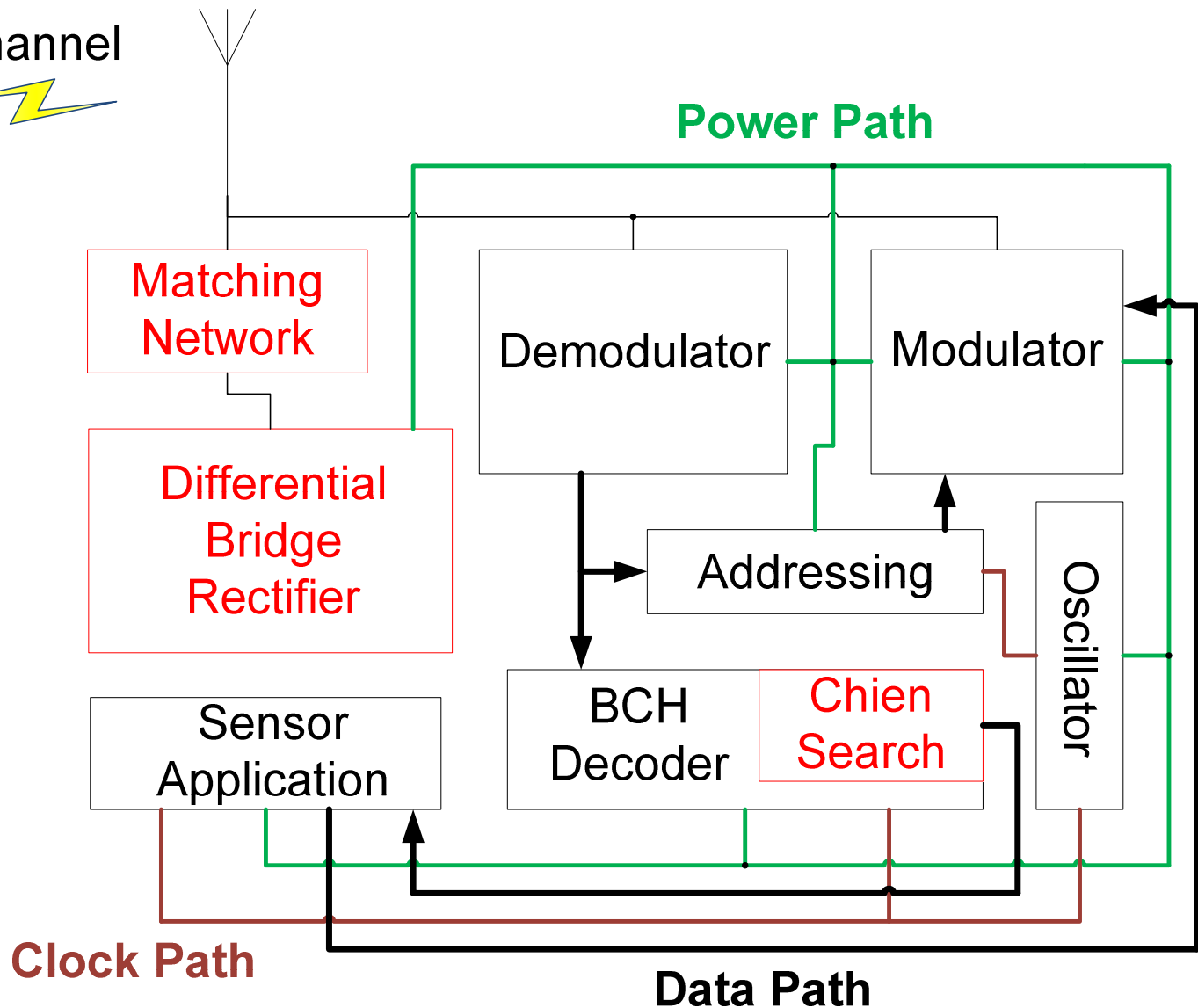




Chien Search and My Contributions

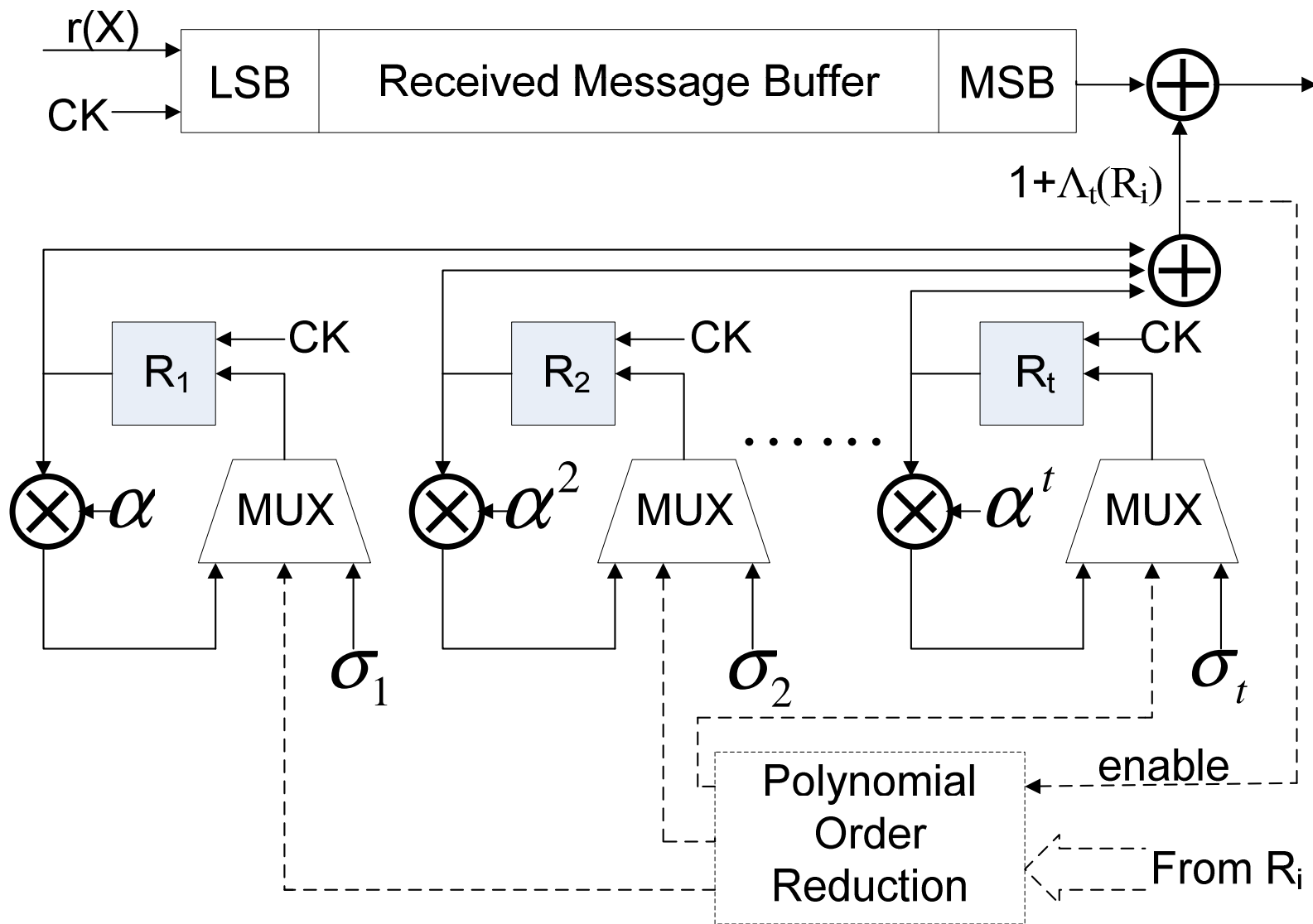- **Chien search** is a popular VLSI circuit for the last decoding step of BCH (Bose-Chaudhuri-Hocquenghem) code, which also consumes the most power
- Proposed a new design strategy for 34% power savings of the circuit
- A paper [1] is published in ISLPED 09
- A journal version is accepted by TVLSI



 The conventional Chien Search (solid line) and the Polynomial Order Reduction (dotted line)



Existing Method: [7]

$$\begin{array}{l}
 \text{Full power: 8 bit-time} \\
 \text{Zero power: 2 bit-time}
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{Full power: 8 bit-time} \\ \text{Zero power: 2 bit-time} \end{array}} \right\} \text{Average power} = \frac{1 \times 8 + 0 \times 2}{10}$$

$$= 0.8$$

Proposed Method:

$$\begin{array}{l}
 \text{Full power: 3 bit-time} \\
 \text{2/3 power: 3 bit-time} \\
 \text{1/3 power: 2 bit-time} \\
 \text{Zero power: 2 bit-time}
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{Full power: 3 bit-time} \\ \text{2/3 power: 3 bit-time} \\ \text{1/3 power: 2 bit-time} \\ \text{Zero power: 2 bit-time} \end{array}} \right\} \text{Average power} = \frac{1 \times 3 + \frac{2}{3} \times 3 + \frac{1}{3} \times 2 + 0 \times 2}{10}$$

$$= \frac{3 + 2 + \frac{2}{3}}{10}$$


$$= \frac{17}{30}$$

$$= 0.56$$

- Our technique is by first making the constant finite-field multipliers (CGFMs) and registers redundant, through Polynomial Order Reduction (POR) before disabling them via clock gating
- On average, for a (n, k, t) BCH code and $\eta = \text{idle/active power for the register}$, the savings becomes:

$$\overline{S_{prop}} \approx 1 - \left[\frac{6n}{3n + 2t + 1} \cdot \left(1 + \frac{t-1}{t+1} \cdot \eta \right) \right]^{-1} \quad (1)$$

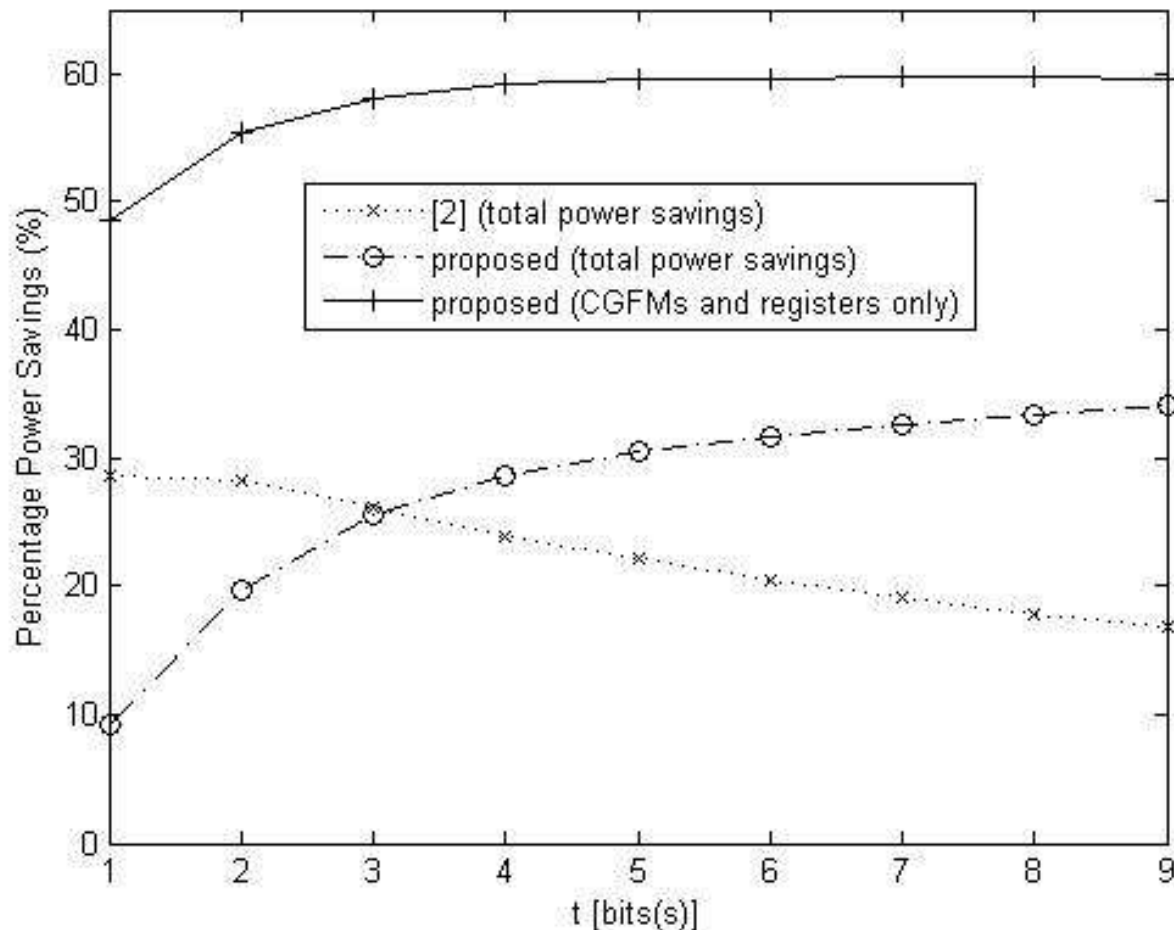- For POR, with u being the highest order of $\Lambda(R)$, we proved that: $R'_w = \sum_{\lambda=w+1}^u R_\lambda$ (2)



- Double the power savings of [2] at $t=9$
- With respect to the conventional circuit, area increase by only 24%, comparing to 106% of the parallel circuit solution [3]

Prior Work for UHF Rectifier

- Many recent work focus on reducing the turn on threshold voltage of transistor in the Dickson Multiplier topology
- These are such as the External V-th Cancellation method (EVC) [9], the Internal V-th (IVC) [8], Self V-th (SVC) [10] and the Zero V-th transistor (ZVT) [5]
- The maximum **P**ower **C**onversion **E**fficiency achieved to date is 37%

Prior Work for UHF Rectifier ..

- [5] identifies leakage as a PCE bottleneck; power optimization \neq that of output voltage
- It is commonly assumed that PCE rises with input voltage [6], and [7] proposed boosting the antenna voltage with L-match
- There is an upper limit in voltage boosting due to bandwidth reduction with increasing Q and [6] proposed higher order matching network for maximizing bandwidth


CMOS Differential Bridge Rectifier

- Implemented in [6] with only PCE of 23%
- Its high PCE potential is rediscovered in 2008 [4]; reported experimental PCE of 66% at input power level of -12dBm
- However, there is no model to support it and it is also not known how a design can be scaled for other load conditions; [4] implies that high PCE is only achievable with high resistance load

Main Contributions

- A complete 4-D DC analysis of differential bridge rectifier is done with MATLAB, using SPICE model data; The resulting PCE contour shows that there exists a maximum achievable PCE, regardless of the loading, and there is an optimal transistor sizes combination for a given tag distance
- A new design scaling strategy for optimal PCE for all possible loading conditions
- An optimal power matching strategy for non-linear load
- A 3-stages rectifier with simulated PCE of 73% and power utilization of 68% at 10m for 915MHz & $P_{EIRP}=4W$

CMOS Differential Half-Bridge

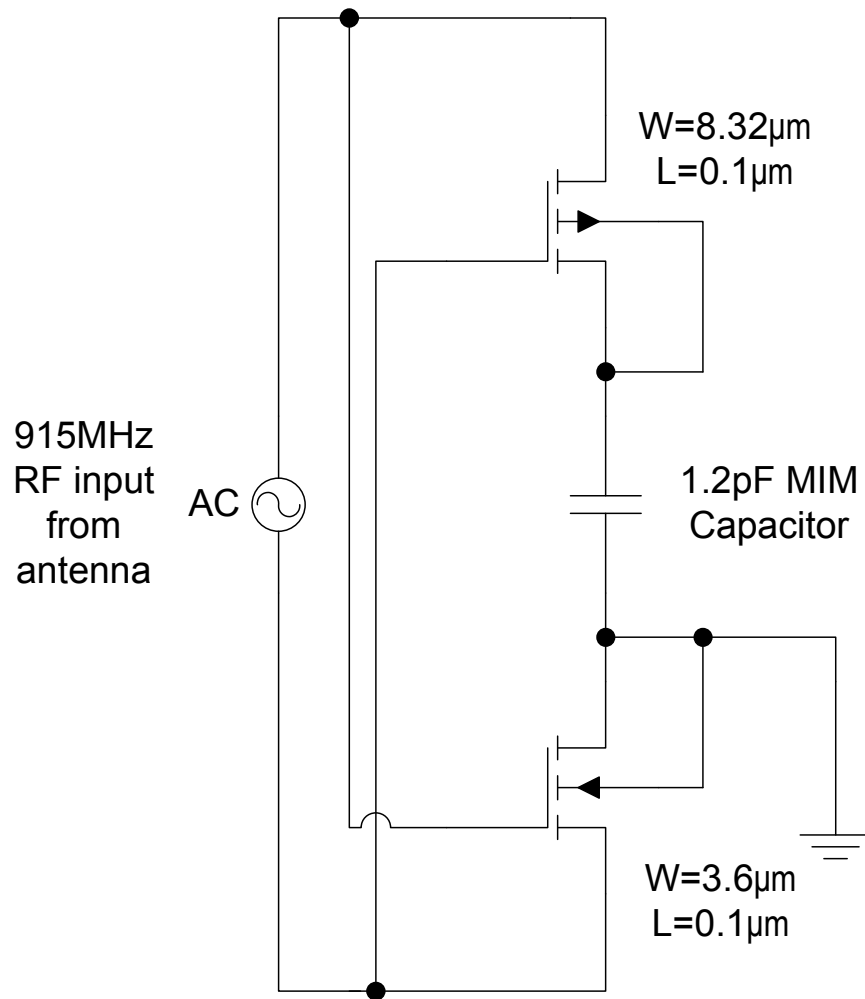


- Operation is rather self explanatory; so, we shall focus only on a few salient pros to the Dickson types
- Input voltage goes fully across V_{gs}
- No charging cycle
- Parasitic current flows through output

CMOS Differential Half-Bridge..

- A more detail investigation reveals that when $V_{in} \geq V_{out}$, the current flows from top to bottom; under this condition, $V_{in} = V_{gsp} = V_{gsn}$ and $V_{in} - V_{out} = V_{dsn} + V_{dsp}$, therefore:
- $[V_{dsp}, V_{dsn}] < V_{in} - V_{out}$. If we set $V_{out} \geq V_{thp}$, the transistors will turn on in triode mode with small on-resistance!!
- During turnoff when $V_{in} < V_{out}$, the conditions are more complicated but we can at least notice that $V_{gsn} = V_{out} + V_{dsp}$, $V_{gsp} = V_{in} - V_{dsp}$, which are decreasing quantities unlike those of the diode-connected FETs used in the Dickson types, which stays constant
- The decreasing V_{gs} offers a much better turn off

Six Regions of Conduction

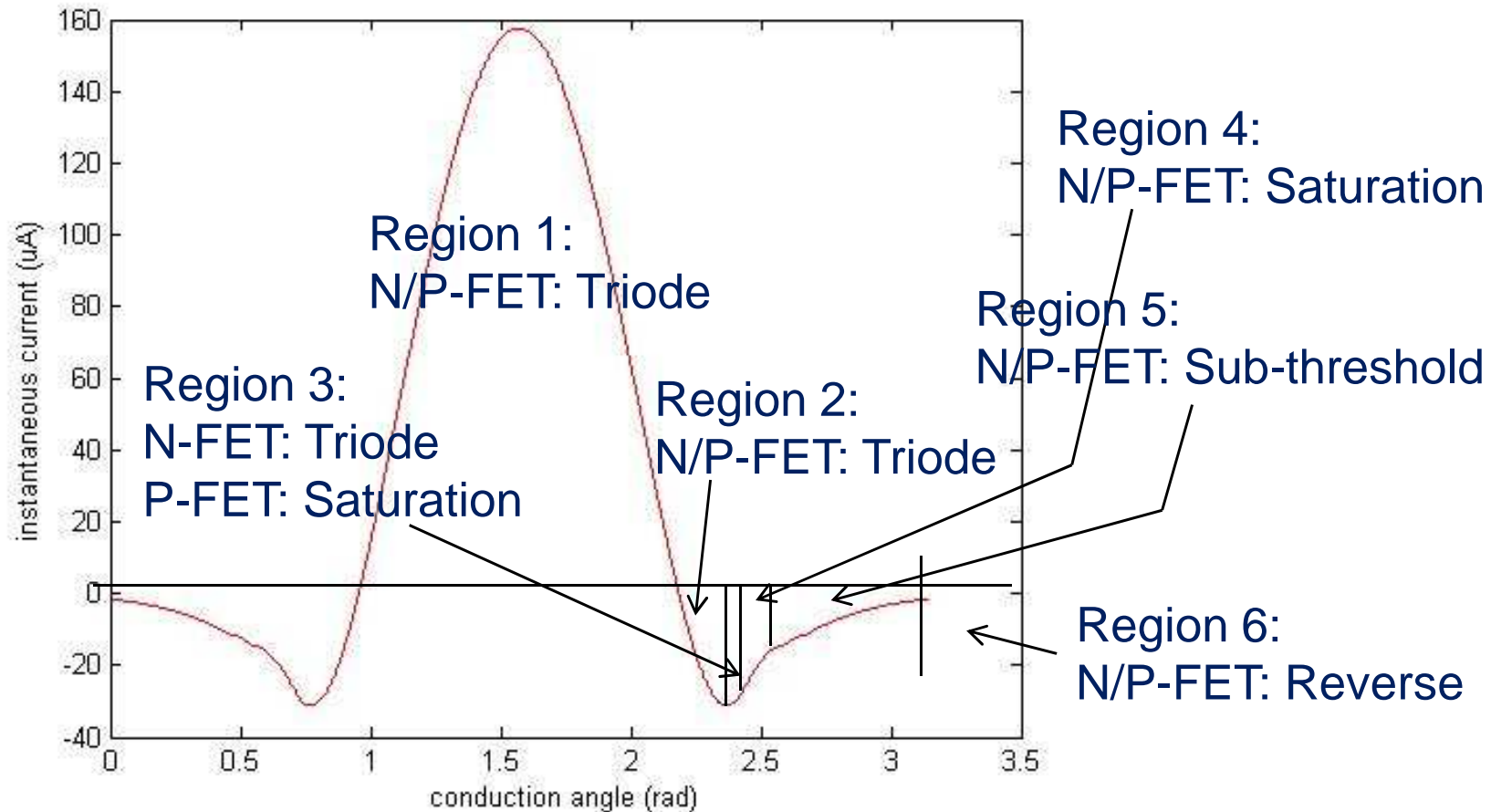Showing here is a sample current waveform in response to one half cycle of a sinusoidal input




- Analysing details of the reverse conduction regions is vital for the understanding of PCE

4-D DC Analysis


- The reverse regions are generally too complicated for analytical solution
- To discover all possible PCE with any transistor combination, we chose to analyse four parameter dimensions
- PCE, V_{out} , g^2 (β_p/β_n) and δ (V_{out}/V_{in})
- This is more than Cadence Spectre can handle, so we wrote a program in MATLAB for the computation

3-D PCE contours

 


Maximum PCE occurs at an unique point

Consequence of Body Effect

 

- Maximum PCE simply shifts to a different point
- Contrary to common assumption, PCE does not decrease but increase !!

Operating with Low V_{out}

 


- Setting V_{out} below V_{thp} , the threshold voltage of P-type transistor, reduces forward current to a size comparable with the reverse current, resulting in low PCE

The 4-th Dimension and Summary

- By varying δ , we get a series of different 3-D contours
- A flat contour corresponds to low δ value and low PCE
- Higher δ values will yield higher PCEs until a point of diminishing return, where the absolute maximum PCE is located; the relative position of max PCE remains static
- Maximum PCE occurs when V_{out} is slightly above V_{thp}
- When V_{thp} is much larger than V_{thn} , increasing the relative size of P-type transistor increases PCE
- Given the same δ , higher V_{sb} improves PCE
- When V_{out} is below or much above V_{thp} , low PCE results
- Actual PCE will be smaller due to neglected AC effects

An Approximated Model

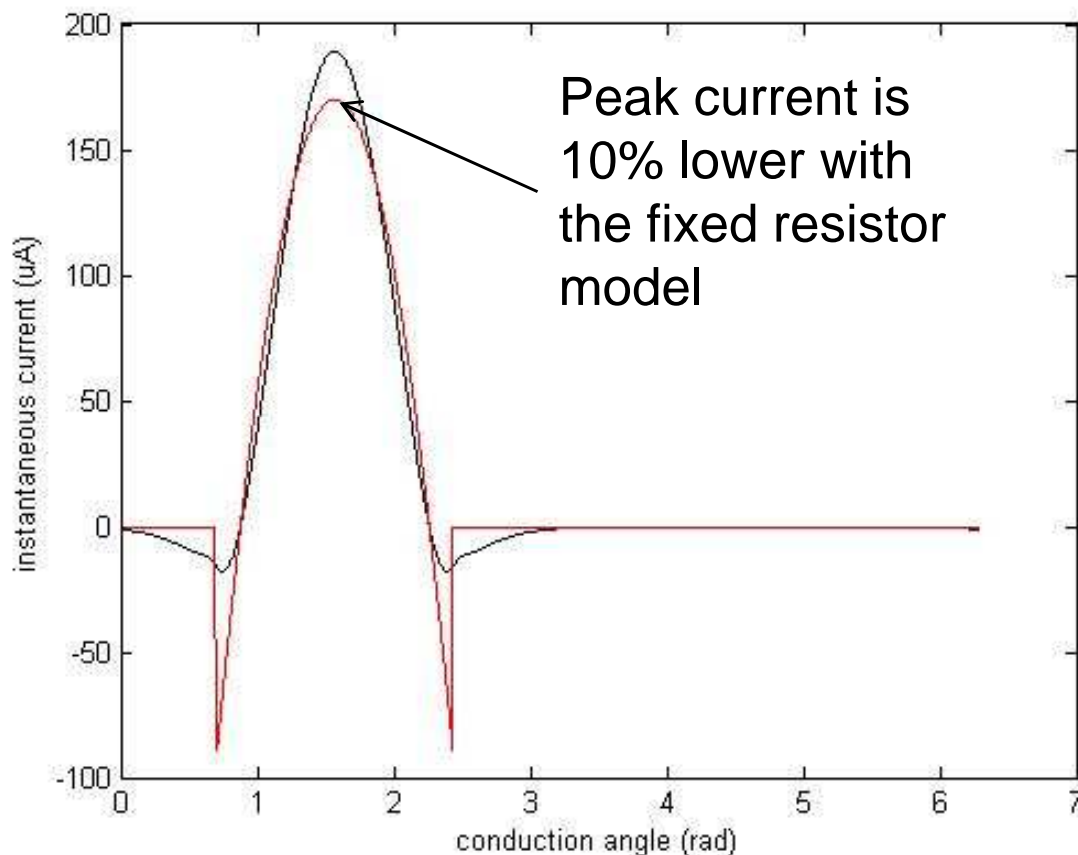

An example for:

$$\delta=0.77$$

$$W_p=31.35\mu\text{m}$$

$$g^2=1.4$$


$$V_{out}=0.33\text{V}$$

$$V_{thp}=0.2785\text{V}$$


$$V_{thn}=0.2806\text{V}$$

This produces an average current of $22.4\mu\text{A}$. A resistor that produces the same current has a value of 579.4Ω

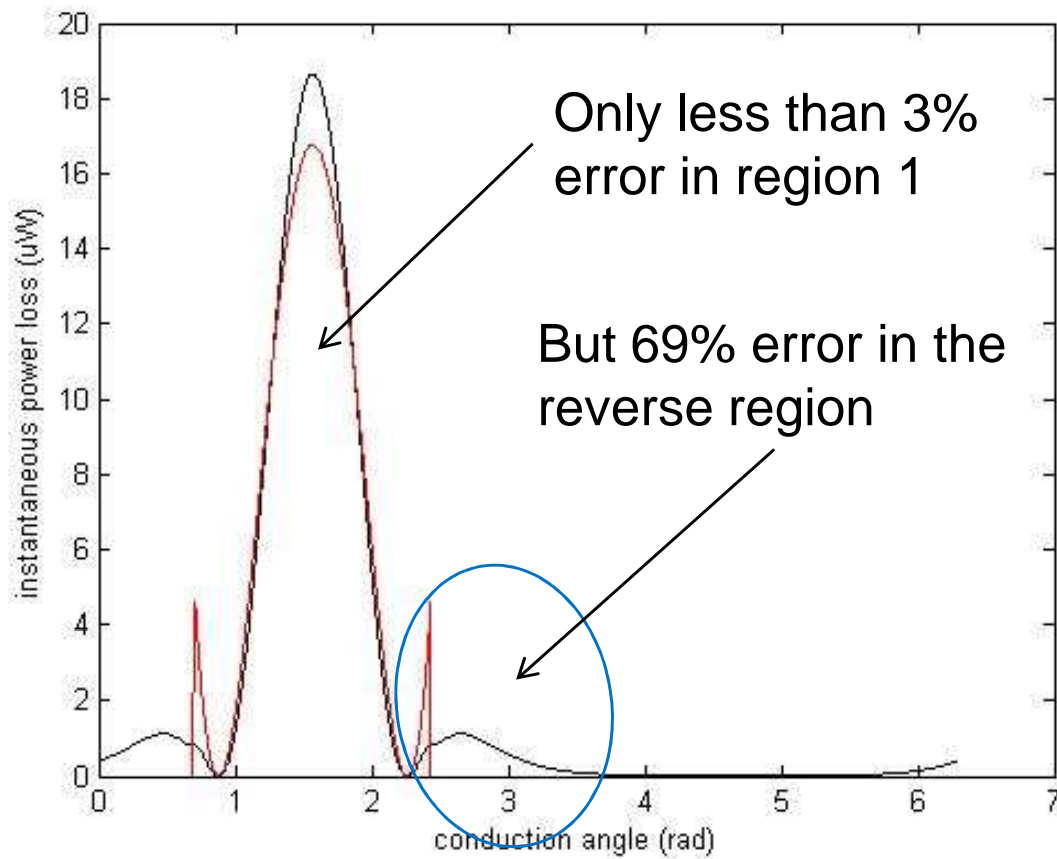- When correctly biased for optimal PCE, the on-region of the transistors behave resistively; could we actually replace it with a fixed value resistor?



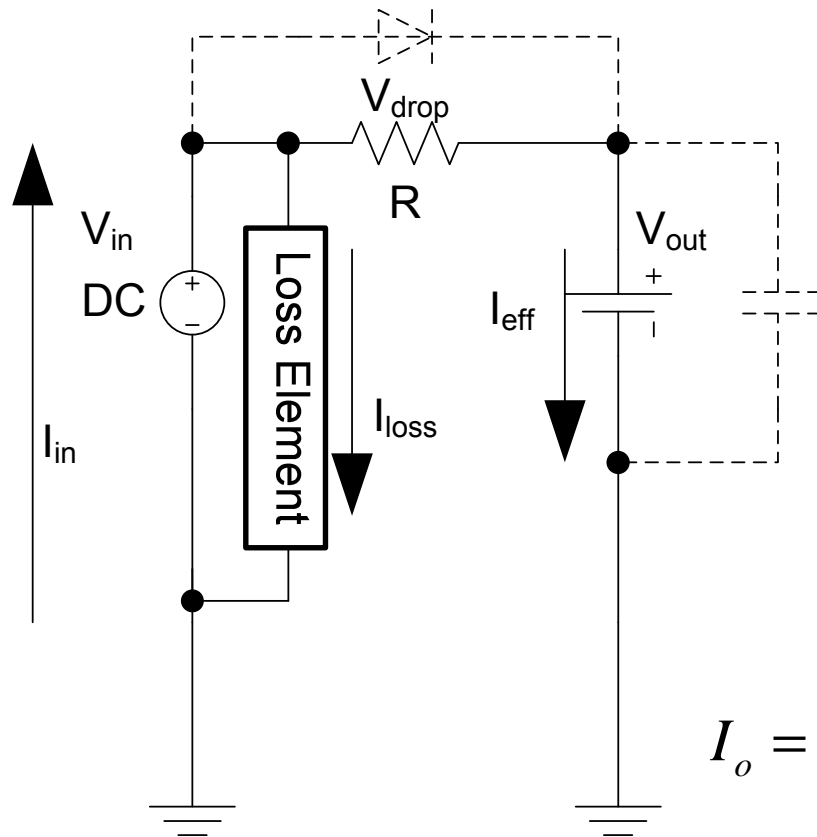- A fixed resistor can sufficiently model region 1
- Since the reverse region loss should be proportional to the forward region loss, we can account for the discrepancy by introducing an equivalent loss resistor




- Assuming a sinusoidal input source, the circuit starts conducting when $V_{in} \cdot \sin(\omega t) > V_{thp}$
- If we further assume that $\delta = V_{out} / V_{in}$ & $\chi = V_{thp} / V_{out}$
- We can show that the average output current I_o :

$$I_o = \frac{V_{in}}{2\pi R} \cdot \left[2\sqrt{1 - (\chi\delta)^2} - \pi\delta + 2\delta \sin^{-1}(\chi\delta) \right] \quad (3)$$

- We can further derive PCE as follows:
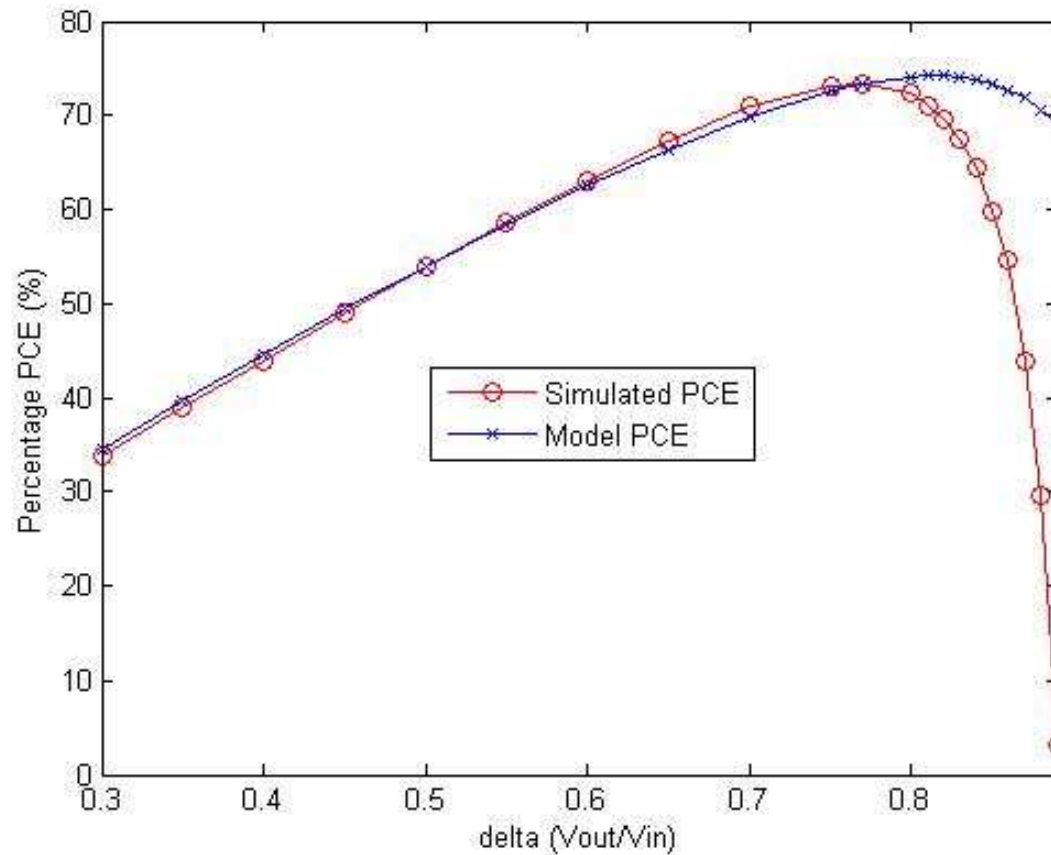
$$PCE = \delta^2 \cdot \frac{\frac{2}{\delta} \sqrt{1 - (\chi\delta)^2} - \pi + 2 \sin^{-1}(\chi\delta)}{\frac{\pi}{2} - \sin^{-1}(\chi\delta) + \delta \cdot (\chi - 2) \cdot \sqrt{1 - (\chi\delta)^2} + \frac{\pi R}{R_{loss}}} \quad (4)$$



An example for:

$$\delta=0.77$$

$$W_p=40.2\mu\text{m}$$

$$G^2=0.6$$

$$V_{out}=0.33\text{V}$$

$$V_{thp}=0.3117\text{V}$$

$$V_{thn}=0.2237\text{V}$$

$$I_o=33.63\mu\text{A}$$

$$PCE=73.33\%$$


$$\text{Effective } R=842.8\Omega$$

$$R_{loss}=135.7\text{K}\Omega$$

- Our model matches the simulated result quite closely up to the maximum PCE of 73.33%
- The model deviates after that point because of the dominance of reverse leakage components

Matching to Non-Linear Load

- The 4-D PCE contour analysis yields area normalized results, we can scale the transistors for the desired operating current without affecting PCE
- Our model equations are useful for generating R and R_{loss} , such that the non-linear rectifier circuit is converted to a piece-wise linear system
- Now, how to match our rectifier to an antenna becomes the issue; prior work assumes a linear model, which is only valid when PCE is low [6]
- But how does it apply to a piece-wise linear system?

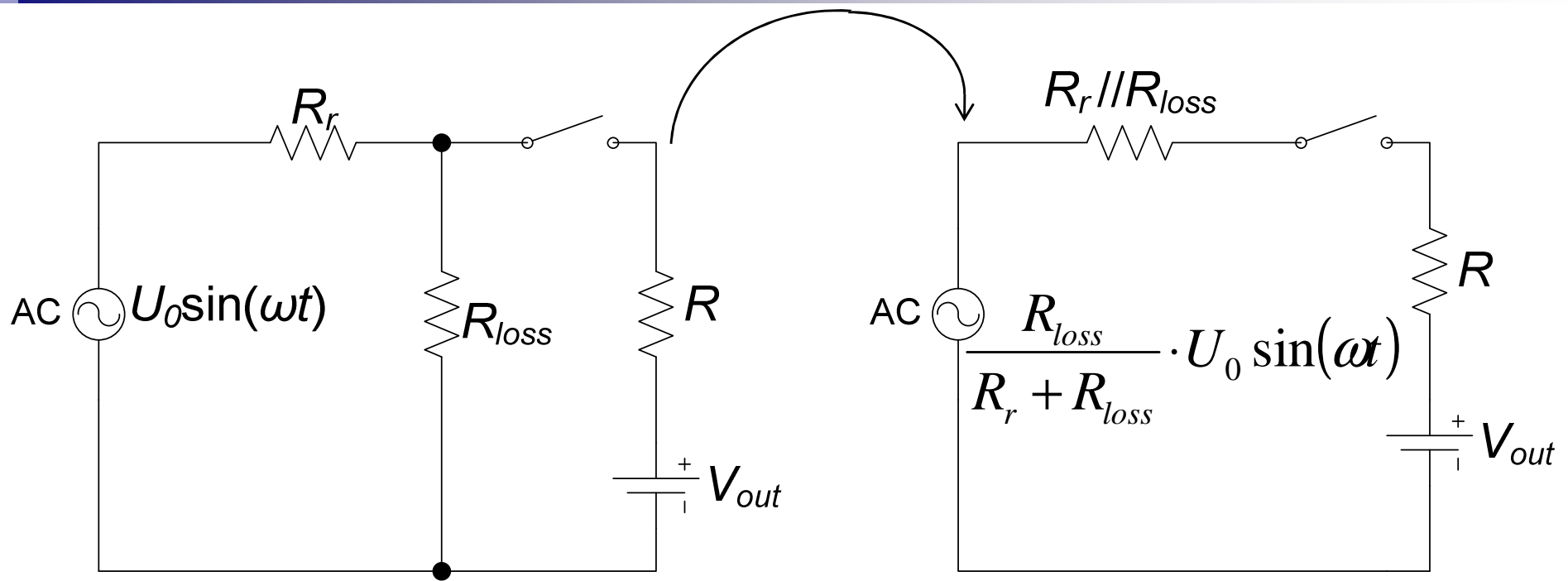

- We may model the antenna and the matching network as an AC signal with an amplitude of U_0 and an effective radiative impedance of R_r ; we may further define k and σ as the following

$$k = \left(1 + \frac{R_r}{R_{loss}} \right) \cdot \frac{V_{out}}{U_0} \quad (5)$$

$$\sigma = \frac{R}{R_r // R_{loss}} = \frac{R \cdot (R_r + R_{loss})}{R_r \cdot R_{loss}} \quad (6)$$

- If P_r is the available power to V_{out} , we show that:

$$P_r = \frac{U_0^2}{8R_r} \cdot \left(\frac{R_{loss}}{R_{loss} + R_r} \right) \cdot \frac{8k}{(1 + \sigma)\pi} \cdot \left[\sqrt{1 - (\chi k)^2} + k \sin^{-1}(\chi k) - \frac{k\pi}{2} \right] \quad (7)$$

- The first term is the available power from the antenna, it is related to the distance from reader by Friis equation

$$P_a = \frac{U_0^2}{8R_r} = \frac{P_{EIRP}}{4\pi r^2} \cdot \frac{\lambda^2}{4\pi} \cdot G \quad (8) \quad U_0 = \frac{\lambda}{2\pi r} \sqrt{2P_{EIRP}GR_r} \quad (9)$$

← wavelength
← Antenna gain

- So, we can define a power utilization factor PU as:

$$PU = \frac{P_r}{P_a} = \left(\frac{R_{loss}}{R_{loss} + R_r} \right) \cdot \frac{8k}{(1 + \sigma)\pi} \cdot \left[\sqrt{1 - (\chi k)^2} + k \sin^{-1}(\chi k) - \frac{k\pi}{2} \right] \quad (10)$$


- PU is a function of k and χ , (assuming R_{loss} , R and σ are known values), differentiating $PU(k)$ lead to:

$$\frac{dPU(k)}{dk} = \sqrt{1 - (\chi k)^2} + 2k \sin^{-1}(\chi k) - k\pi + (1 - \chi) \cdot \frac{\chi k^2}{\sqrt{1 - (\chi k)^2}} \quad (11)$$

- maximum power utilization can be founded by setting the equation to zero and then solving it
- For the special case when $\chi=1$, maximum PU for a full-wave bridge rectifier occurs when $k=0.3942$ at a value of **0.9226**
- Therefore, maximum available power to the rectifier's output does not equal P_a , but $0.9226P_a$ and it does not occur when V_{out} of each stage is equal to half of the input voltage but:

$$V_{out} = 0.3942 \left(\frac{R_{loss}}{R_{loss} + R_r} \right) \cdot U_0 \quad (12)$$

Design of Multistage Rectifier

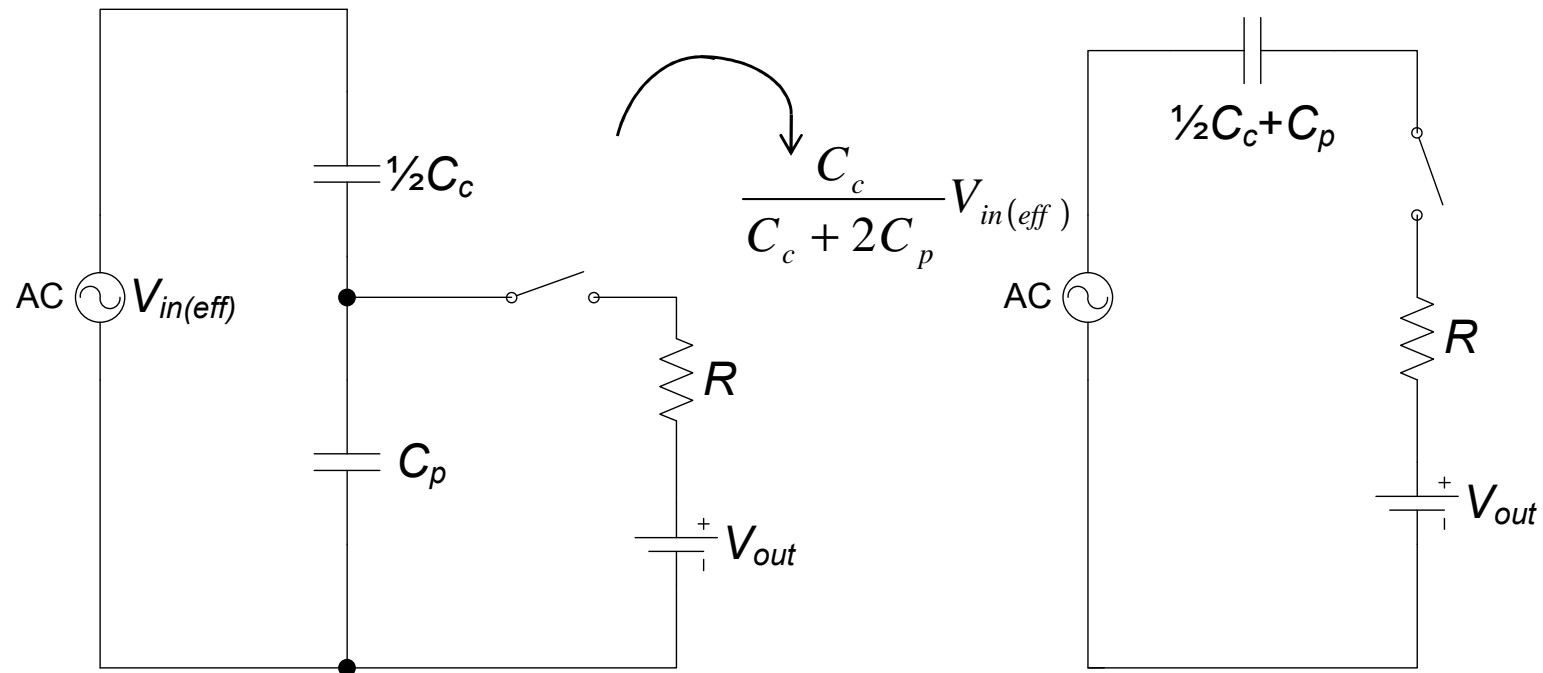

- There is a parasitic capacitance C_p across the load
- And we need coupling capacitor C_c for multistage

- Simple impedance calculation cannot be directly applied as the switching introduces discontinuity
- However, this is nothing more than Laplace transform with some initial conditions at the point of switching; the current through V_{out} is shown to be:

$$i(t) = K_1 \sin(\omega t + \theta + \alpha) + K_2 e^{-\frac{2t}{R \cdot (C_c + 2C_p)}} \quad (13)$$

- Where:
$$K_1 = \frac{\omega C_c}{\sqrt{4 + [\omega R (C_c + 2C_p)]^2}} \cdot V_{in(eff)} \quad (14)$$

$$\alpha = \frac{\pi}{2} - \tan^{-1} \left[\frac{\omega R (C_c + 2C_p)}{2} \right] \quad (15) \quad \theta = \sin^{-1} \left[\frac{(V_{thp} - \Delta V_c)(C_c + 2C_p)}{V_{in(eff)} \cdot C_c} \right] \quad (16)$$

$$K_2 = \frac{V_{thp} - V_{out}}{R} - K_1 \sin^{-1}(\theta + \alpha) \quad (17)$$

- There is charge loss through the equivalent capacitor during the switching that occurs on every cycle, these charge loss caused a voltage drop V_{dt}

$$V_{dt} = \frac{I_{load(total)}}{f \cdot (C_c + 2C_p)} \quad (18)$$

- For fullwave rectifier, during steady state, the initial voltage at the capacitor becomes:

$$\Delta V_c = \frac{V_{dt}}{2} \quad (19)$$

- Which means although there is a voltage drop, the initial DC offset keeps the amplitude of the signal seen by R and V_{out} almost exactly the same before and after switching; there is only a phase shift involved

- The current through C_c can be found from $i(t)$, which could then be used for determining the effective V_{out}
- The effective R can be calculated by recognizing the tap-capacitor matching circuit

$$R_{eff} = \frac{1+Q^2}{1+Q_2^2} (R // R_{loss}) \quad (20) \quad Q_2 = \omega C_p (R_{loss} // R) \quad (21)$$

$$Q = \frac{1}{\left[\frac{1}{2} C_c // \left(\frac{1+Q_2^2}{Q_2^2} C_p \right) \right]} \cdot \frac{R // R_{loss}}{1+Q_2^2} \cdot \omega \quad (22)$$


- The reactive current due to C_c and C_p can be cancelled with an in-parallel inductor; the low Q due to the polysilicon gates can be relieved by multiple fingers
- Finally, we need to determine the required R_r

- It can be shown that:

$$\sigma = \frac{k(1-\delta)}{\delta-k} \quad (23)$$

$$R_r = \frac{R_{eff} \cdot R_{loss}}{\sigma \cdot R_{loss} - R_{eff}} \quad (24)$$

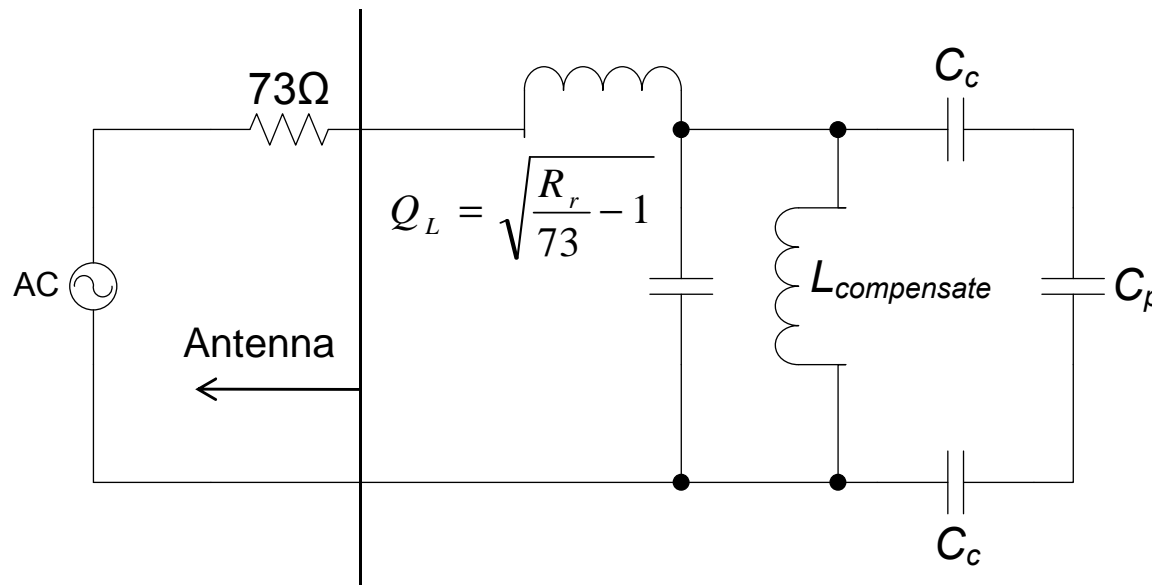- Typically, low cost antenna has simple design with low impedance, such as dipole antenna with an impedance of 73Ω ; L-match may be used to convert 73Ω to R_r



- Maximum power utilization rules imply that effective V_{out} for each stage should be the same

- Since V_{out} also fixes U_o , it implies maximum PU only at one distance. Reversely speaking, it means that, for any given distance, there exists an optimal transistor size
- With these design rules, we came up with a 3-stages full-wave differential bridge rectifier circuit, results follows:

r(m)	Pa (μ W)	Pa (dBm)	PU	PCE	Io (μ A)
5	178.38	-7.49	0.6399	0.6982	115.3
7	91.01	-10.41	0.7174	0.7267	65.95
9	55.06	-12.59	0.7099	0.7405	39.48
10	44.59	-13.51	0.6795	0.7382	30.61
11	36.86	-14.34	0.6294	0.7336	23.43
12	30.97	-15.09	0.5626	0.7165	17.6
13	26.39	-15.79	0.4806	0.6851	12.81

Conclusions

- Developed a complete design methodology for differential bridge rectifier
- Shown that a different optimal power transfer equation applies to this rectifier
- Shown that there is an optimal transistor size for a target distance
- And that body-effect and high output current will not necessarily degrade PCE
- Simulated a design with PCE of 73% & PU of 67% at 10m and P_{EIRP} of 4W

Reference

1. S.Wong, C.Chen, Q.M.J. Wu, "Power-Management-Based Chien Search for Low Power BCH Decoder," International Symposium on Low Power Electronics and Design, 2009, ISLPED 2009, Aug 19-21, 2009
2. Y. Wu, "Low power decoding of BCH codes," IEEE International Symposium on Circuits and Systems, ISCAS 2004, vol. 2, May 2004, pp. II-369-372.
3. A. Raghupathy and K. J. R. Liu, "Algorithm-based low-power/high-speed Reed-Solomon decoder design," IEEE Trans. on Circuits and Systems—II: Analog and Digital Signal Processing, vol. 47, no. 11, Nov. 2000, pp. 1254-1270.
4. A. Sasaki, K. Kotani, T. Ito, "Differential-Drive CMOS Rectifier for UHF RFIDs with 66% PCE at -12dBm Input," IEEE Asian Solid-State Circuits Conference, 2008, A_SSCC'08, 3-5 Nov, 2008, pp. 105-108
5. J. Yi, W. Ki, C. Tsui, "Analysis and Design Strategy of UHF Micro-Power CMOS Rectifiers for Micro-Sensor and RFID Applications", IEEE Trans. on Circuits and Systems-I: Regular Papers, Vol. 54, No.1, January 2007, pp.153-166

6. S. Mandal, R. Sarpeshkar, “Low-Power CMOS Rectifier Design for RFID Applications”, IEEE Trans. on Circuits and Systems-I:Regular Papers, Vol. 54, No.6, June 2007, pp. 1177-1188
7. A. Shameli, A. Safarian, A. Rofougaran, et al., “Power Harvester Design for Passive UHF RFID Tag Using a Voltage Boosting Technique”, IEEE Trans. on Microwave Theory and Techniques, Vol. 55, Issue 6, Part 1, June 2007, pp.1089-1097
8. H. Nakamoto, D. Yamazaki, T. Yamamoto, H. Kurata, S. Yamada, K. Mukaida et al., “A Passive UHF RF Identification CMOS Tag IC Using Ferroelectric RAM in 0.35- μm Technology”, IEEE Journal of Solid-State Circuits, Vol. 42, No.1, January 2007, pp. 101-110
9. T. Umeda, H. Yoshida, S. Sekine, Y. Fujita, et al., “A 950-MHz Rectifier Circuit for Sensor Network Tags With 10-m Distance”, IEEE Journal of Solid-State Circuits, Vol. 41, No. 1, January 2006, pp. 35-41
10. K. Kotani, T. Ito, “High Efficiency CMOS Rectifier Circuit with Self-V_{th}-Cancellation and Power Regulation Functions for UHF RFIDs”, IEEE Asian Solid-State Circuits Conference 2007, ASSCC 07, Nov. 07, pp. 119-122
11. C. Ma, C. Zhang, Z. Wang, “Power Analysis for the MOS AC/DC Rectifier of Passive RFID Transponders”, IEEE Asia Pacific Conference on Circuits and Systems 2006, APCCAS 2006, Dec. 06, pp.1350-1353

Endorsements

- These work were funded by the AUTO21 Network of Centres of Excellence, Canada





Questions?